

A student performs an experiment to determine the relationships among voltage, current, and resistance. The student's procedure includes the following steps:

- Connect a 3.0 V battery to a $42\ \Omega$ resistor.
- Measure the current using an ammeter and record the value.
- Replace the $42\ \Omega$ resistor with a $54\ \Omega$ resistor, and then with a $66\ \Omega$ resistor, measuring and recording the current for each resistor.

The table below shows the data collected.

Student's Data

Resistance (Ω)	Current (A)
42	0.071
54	0.056
66	0.045

- In your Student Answer Booklet, draw a schematic diagram of the student's original circuit with the $42\ \Omega$ resistor. Be sure to label the battery and the resistor.
- Describe in words the relationship between current and resistance as voltage is held constant.

The student will investigate these relationships further using a different experiment.

- Write a procedure the student could use to test the relationships among voltage, current, and resistance if the only materials available for use are three 3.0 V batteries, one $30\ \Omega$ resistor, wire, and an ammeter.
- In your Student Answer Booklet, make a data table similar to the Student's Data table above to show the expected current measurements for your procedure from part (c). Show your calculations and include units in your answer.