

13

A light bulb with a potential difference of 120 V across it carries a current of 1.5 A. Which of the following is the power consumption of the light bulb?

A. 0.013 W

B. 80 W

C. 120 W

D. 180 W