

16

What is the current flowing through a 60 W light bulb when it is connected to a 120 V source?

A. 0.5 A

B. 2.0 A

C. 180 A

D. 7800 A