

20

A circuit has a light bulb connected to a constant voltage source. Which of the following changes must increase the power in the circuit?

- A. using a light bulb that is more efficient
- B. using a light bulb that draws more current
- C. using a light bulb that is rated to last longer
- D. using a light bulb that has a larger resistance