

45

A student connects a small solar panel to a $40\ \Omega$ resistor to make a simple circuit. The solar panel produces a voltage of $2\ \text{V}$.

- Identify a different circuit component that could serve the same purpose as the solar panel in this circuit.
- Calculate the current in the student's circuit. Show your calculations and include units in your answer.
- Calculate the power produced by the student's circuit. Show your calculations and include units in your answer.
- Describe one way the student can modify the circuit to increase the current through the resistor.