
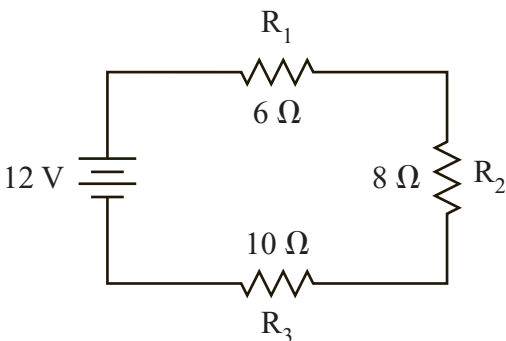


Two circuits, W and X, are shown in the diagrams.

Circuit W

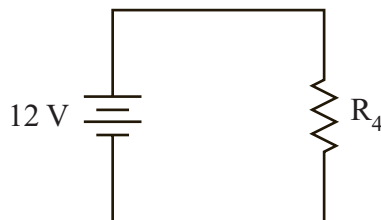

Circuit X




Circuit X has the same total resistance as circuit W, but circuit X has only one resistor, R_4 .

- Calculate the resistance of R_4 . Show your calculations and include units in your answer.
- Calculate the current through R_4 . Show your calculations and include units in your answer.

Another circuit, Y, has the same battery and resistor as circuit X but also has another resistor, R_5 , as shown.

Circuit Y

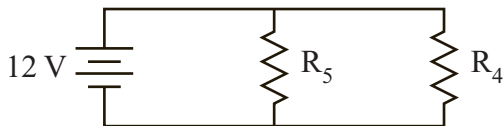

- Determine whether adding R_5 increases or decreases the total current in circuit Y. Explain your reasoning.
- In your Student Answer Booklet, copy circuit Y. On your circuit, add a third resistor labeled " R_{new} " in a location that will **not** change the current through R_4 .